

# 2CV BATTERY CHARGING CIRCUIT

Revision 3



By Graeme Dennes


## 2CV BATTERY CHARGING CIRCUIT

Revision 3

By Graeme Dennes

This article describes the battery charging arrangements used in a 2CV fitted with an alternator. The 2CV charging system consists essentially of the battery, the voltage regulator and the alternator. The whole purpose of these three components is to keep the battery in a fully charged state and to maximise the life of the battery. Although charging circuits in general can often be quite complex, there are in fact very few components involved in the 2CV charging circuit, as Figure 1 below shows. It is the simplest possible arrangement.

### 2CV CHARGING CIRCUIT

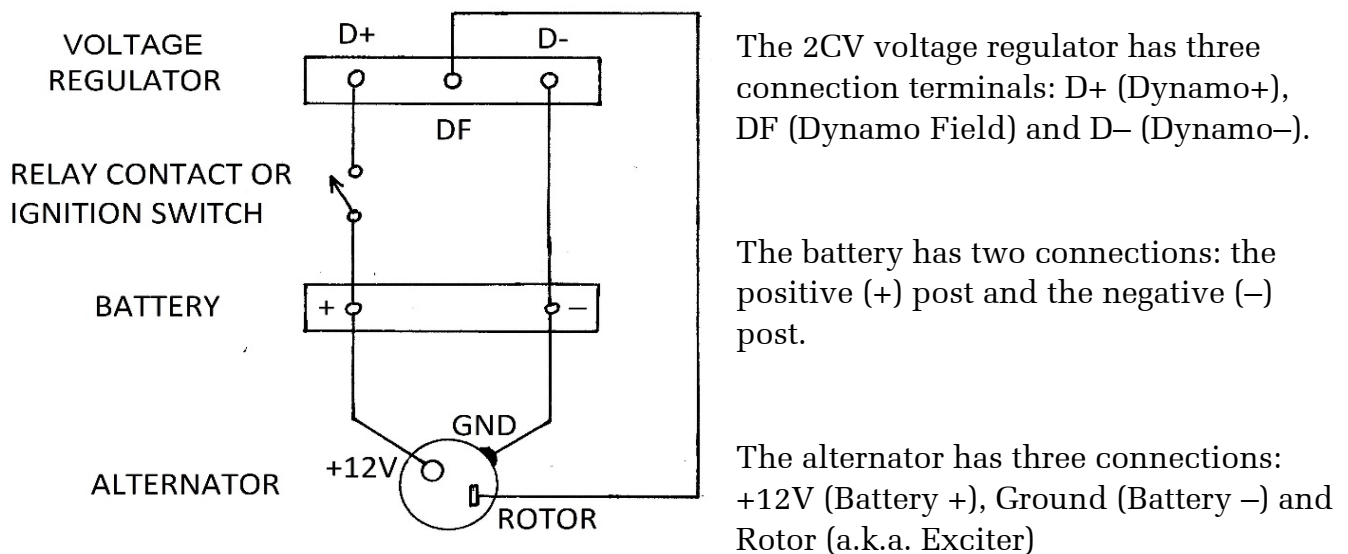

*Fig. 1*

When the ignition switch is ON, the regulator's D+ terminal is connected to the battery + post via either a relay contact (if a relay is fitted) or via the ignition switch.

#### Voltage Regulator:

The purpose of the voltage regulator is to maintain a constant voltage across the battery posts at all driving times, irrespective of engine speed, electrical loading on the battery or state of charge of the battery. The voltage is maintained at the regulator's voltage set point.

#### Voltage Set Point:

The voltage set point is a design parameter of a voltage regulator. It is the voltage which the regulator aims to maintain across the battery posts. We'll consider the application of the Bosch RE57 voltage regulator as an example. This regulator has a voltage set point of 14.2V, which is the optimum charging voltage for the standard lead-acid battery, i.e., the optimum voltage to maintain across the battery posts during vehicle operation. The job of the regulator is to maintain that voltage across the battery posts.



Fig. 2 2CV Alternator

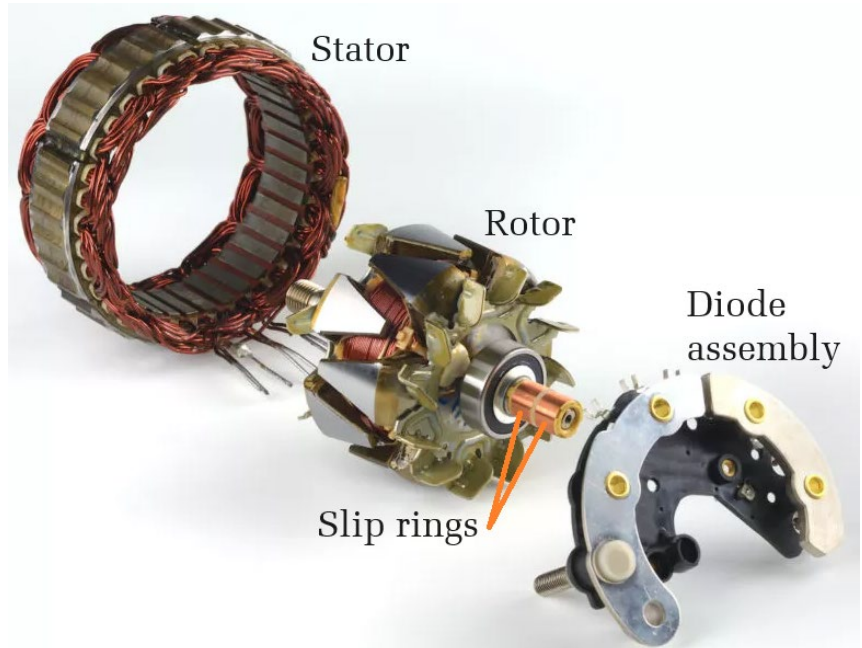


Fig. 3 Alternator internals

#### Circuit Operation:

The voltage across the battery is controlled by the alternator, the alternator voltage is controlled by the regulator, and the regulator is controlled by the battery voltage! It's an automatic level control function operating within a feedback loop.

During vehicle operations, the voltage regulator is continually sensing the battery voltage across its D+ and D- terminals and comparing it with its voltage set point. If the voltage regulator senses that the battery voltage is lower than the voltage set point, i.e., lower than 14.2V, which happens when, say, the headlights are turned on and the battery voltage drops a little due to the headlight current, the voltage regulator responds by increasing the control voltage at its DF terminal. This increases the voltage at the alternator rotor terminal, which causes the alternator's output voltage to rise, which increases the voltage across the battery posts and across the regulator's D+ and D- terminals, until the battery is (again) being charged at the optimum voltage (the voltage set point) of 14.2V as sensed by the regulator's D+ and D- terminals.

Conversely, if the regulator senses that the battery voltage is higher than the voltage set point, which happens when, say, the headlights are switched off and the battery voltage rises a little, the voltage regulator responds by decreasing the control voltage at its DF terminal. This decreases the voltage at the alternator rotor terminal, which causes the alternator's output voltage to decrease, which decreases the voltage across the battery posts and across the regulator's D+ and D- terminals, until the battery is (once again) being charged at the optimum voltage of 14.2V as sensed by the regulator's D+ and D- terminals.

This is the fundamental way the battery, the alternator and the voltage regulator operate to maintain the optimum voltage across the battery posts to maximise the life of the battery.

As a simple check, with a fully charged battery, if the engine speed is increased to perhaps two thousand (or higher) RPM, a multimeter connected *directly across the battery posts* will measure a DC voltage equal to the regulator's voltage set point, i.e., a DC voltage of 14.2V. *At no time should the battery voltage rise above the regulator's voltage set point of 14.2V, regardless of engine RPM.* If it does, something is very wrong.

In summary, that's how the voltage regulator operates to exercise control over the alternator output voltage so the battery is always being optimally charged. It's all accommodated automatically by the voltage regulator. It's also conditional upon the voltage regulator operating to its specifications and the integrity of the wiring and the wiring connections, including crimp connectors.

Any failings within the wiring connections or any additional circuit resistances in the wiring at Figure 1 *will* result in battery and battery charging problems, including an overcharged battery! Dead set! Refer to the writer's article, *2CV Battery Problems Solved* for further information on ensuring the voltage across the battery posts never rises above the voltage set point of the regulator (14.2V).

## LIST OF ARTICLES BY THE WRITER

1. 2CV 40-Litre Fuel Tank (Revision 1)
2. 2CV API GL-4 Gearbox Oil (Revision 3)
3. 2CV Battery Charging Circuitry (Revision 3)
4. 2CV Battery Problems Solved (Revision 7)
5. 2CV Brake Saga (Revision 1)
6. 2CV Buyer's Questions (Revision 2)
7. 2CV Carburettor Cover Screws (Revision 1)
8. 2CV Carburettor Jets and Adjustments (Revision 1)
9. 2CV Engine Problems (Revision 6)
10. 2CV Fuel Filter (Revision 1)
11. 2CV Fuel Gauge and Battery Meter (Revision 1)
12. 2CV Gearbox Output Hubs (Revision 2)
13. 2CV Gearbox Unwinding Debacle
14. 2CV Hard Luck Stories (Revision 2)
15. 2CV Headlights Improvement (Revision 4)
16. 2CV Ignition Coil (Revision 6)
17. 2CV Knife Edges Replacement (Revision 3)
18. 2CV Low Oil Pressure Beeper and Lights On Beeper (Revision 1)
19. 2CV Maintenance - Part 1 of 2 (Revision 18)
20. 2CV Maintenance - Part 2 of 2 (Revision 18)
21. 2CV Oil Breather (Revision 5)
22. 2CV Oils and Maintenance Advice From Burton (Revision 3)
23. 2CV Points Ignition Reinstallation (Revision 1)
24. 2CV Roof Rack (Revision 3)
25. 2CV Secondary Choke Butterfly Adjustment (Revision 4)
26. 2CV Spare Parts to Carry (Revision 5)
27. 2CV Valve Clearance Adjustment (Revision 2)
28. Better Fuel Hose Clamps (Revision 1) – **applies to all vehicle brands**
29. Better UHF CB Car Radio Performance (Revision 7) – **applies to all vehicle brands**
30. Ignition Coil Ballast Resistors (Revision 5) – **applies to all vehicle brands**
31. The Workshop (Revision 3) – **applies to all workshops and all vehicle brands**

## FINAL STATEMENT

My acknowledgement and grateful appreciation is given to the web sites from which photos/drawings/diagrams have been sourced.

If material copyrighted by others has been inadvertently used in this document without permission, then upon receiving advice, the writer will remove the material immediately.

This article may be updated in the future and assigned a new revision number.

Before using the information in this article, ensure the latest revision is being used.

If you have questions about the information in this article, if you find errors or incorrect statements, if you have suggestions for improvement, or should you wish to republish this article in your club magazine, please - contact the writer at: [gdennes@gmail.com](mailto:gdennes@gmail.com)

The hosting or republishing of this article without the formal consent of the writer is not authorised and will constitute an infringement of copyright.

Copyright © Graeme Dennes 2021